



AMERICAN INTERNATIONAL UNIVERSITY – BANGLADESH


Where leaders are created

Control Logic Design

[Ch # 10]

Introduction

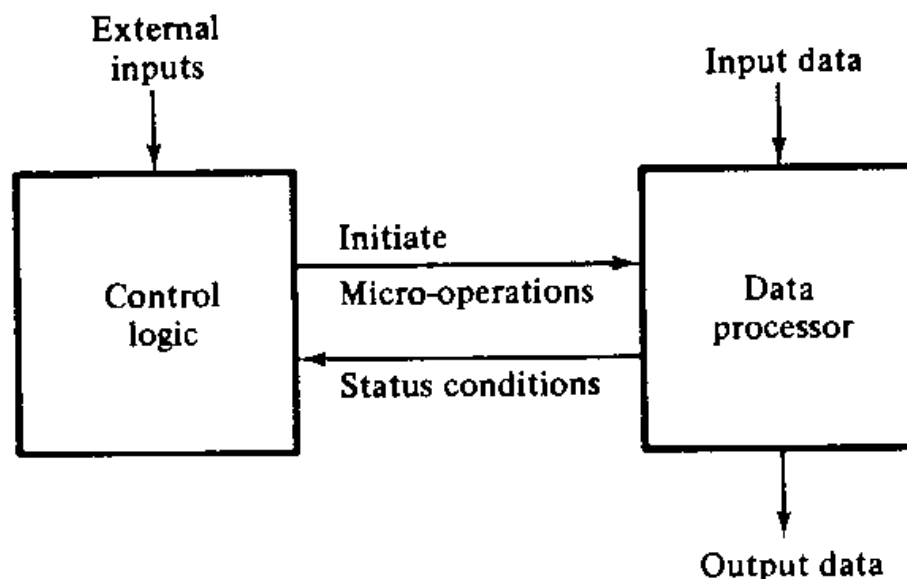- The process of **logic design** is a **complex** undertaking.
- The relationship between the control and the data processor in a digital system is shown in below figure.
- The data processor part may be general purpose processor unit or it may consist of individual registers.
- The **control** initiates all **microoperations** in the data processor.



Control Organization


Once a **control sequence** has been established, the **sequential** system that implements the control operations must be designed.

- Methods of Control Organization (4 methods)
 - One flip-flop per state method
 - Sequence register and decoder method
 - PLA control
 - **Microprogram control**
- The first two methods must use SSI and MSI circuits for the implementations.
- PLA or **Microprogram** uses an **LSI** device.

N.B: VLSI (Very large scale integration) Millions of transistors are integrated on a single silicon chip whereas in **LSI (large scale integration)** a few thousands of transistors are integrated on a single silicon chip

Microprogram Control

 - The **Purpose** of the control unit is to initiate a series of **sequential steps of microoperations**.
- A control unit whose control variables are stored in a **memory** is called a **microprogrammed control unit**.
- Each control word of memory is called a **microinstruction**.
- A sequence of microinstructions is called a **microprogram**.



Hard-wired Control -Example

- The design is carried out in five consecutive steps
 1. The problem is **stated**
 2. An initial **equipment configuration** is assumed
 3. An **algorithm** is formulated
 4. The **data-processor** part is specified
 5. The **control logic** is designed


1. Statement of the problem

- Addition and subtraction of binary fixed point numbers when **negative** numbers are in sign **2's** complement form.
- The addition of two numbers stored in registers of finite length may result in a sum that exceeds the storage capacity of the register by one bit.
- The **extra bit** is said to cause an **overflow**.

+ 6	0 000110		- 6	1 111010
		+		+
+ 9	0 001001		+ 9	0 001001
+ 15	0 001111		+ 3	0 000011
+ 6	0 000110		- 9	1 110111
		+		+
- 9	1 110111		- 9	1 110111
- 3	1 111101		- 18	1 101110

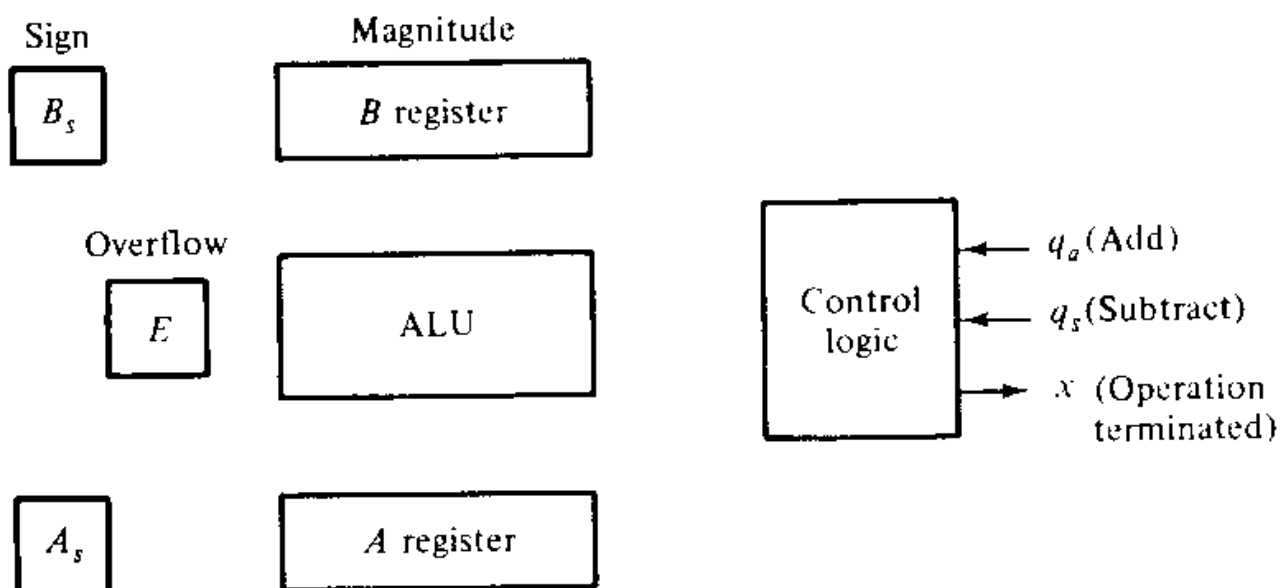2. Equipment Configuration

- The two signed binary numbers to be added or subtracted contains n bits.
- The magnitudes of numbers contain $k=n-1$ bits are stored in registers A and B.
- The **sign bits** are stored in **Flip Flops** As and Bs.



Register configuration for the Adder-subtractor

3. Derivation of the Algorithm

- When the numbers are added or subtracted algebraically, there are **eight** different conditions to be considered and may be expressed as compact form as follows:

$$(\pm A) \pm (\pm B)$$

- In arithmetic operation specified in **subtraction**, we **change the sign of B and add**. So the relationships :

$$(\pm A) - (+B) = (\pm A) + (-B)$$

$$(\pm A) - (-B) = (\pm A) + (+B)$$

- This reduces the **number of possible** conditions to **four**, namely:

$$(\pm A) + (\pm B)$$

3. Derivation of the Algorithm cont....

- When the signs of **A** and **B** are the **same**, we **add** the two magnitudes and the **sign of the result** in the **same** as the **common sign**.
- When the sign of **A** and **B** are **not same**, we **subtract** the smaller number from the larger and the **sign of the result** is the sign of the larger number.

	<u>if $A \geq B$</u>	<u>if $A < B$</u>
$(+A) + (+B) =$	$+(A + B)$	
$(+A) + (-B) =$		$+(A - B) = -(B - A)$
$(-A) + (+B) =$		$-(A - B) = +(B - A)$
$(-A) + (-B) =$	$-(A + B)$	


Flowchart for sign magnitude addition and subtraction

An operation is initiated by either input q_s or input q_a . Input q_s initiates a subtraction operation, so the sign of B is complemented. Input q_a initiates an add operation and the sign of B is unchanged. The next step is to compare the two signs. The decision block marked with $A_s:B_s$ symbolizes this decision. If the signs are equal, we take the path marked by the symbol $=$. Otherwise, we take the path marked by \neq .

For equal sign, the contents of A is added to the contents of B and the sum is transferred to A. The value of the **end carry** in this case is an **overflow**, so the E flip flop is made equal to output carry C_{out} . The circuit then goes to its initial state and output becomes 1. The **sign of the result** in this case is the same as the **original sign of A_s** so the sign bit is left unchanged.

Rough

$$A - B = A - (+B) \\ = A + (-B)$$

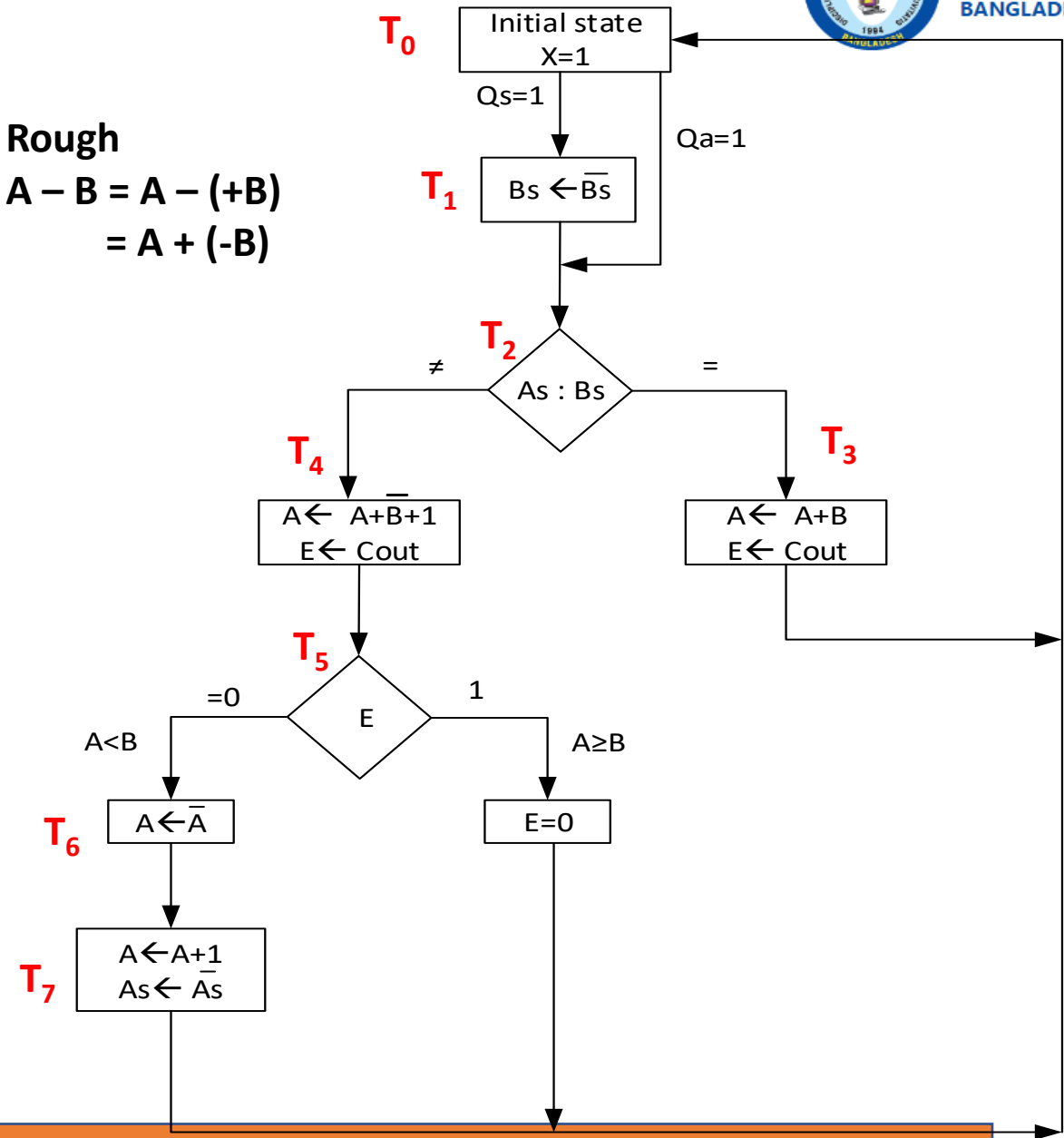

Flowchart for sign magnitude addition and subtraction contd..

The two magnitudes are **subtracted** if the signs are not the same. The subtraction of the magnitudes is done by adding A to the 2's complement of B. No overflow can occur if the numbers are subtracted, so E is cleared to 0. A '1' in E indicates that $A > B$ and the number in A is the correct result. The **sign of the result** again is equal to the **original value of As**. A '0' in E indicates that $A < B$. For this case, it is necessary to form the 2's complement of the value in A and complement the sign in As. The 2's complement of A can be done with one microoperation, $A \leftarrow A' + 1$. However, we want to use the previously designed ALU which does not have the 2's complement operation. For this reason, the 2's complement is obtained from the complement and increment operations which are available in the ALU.

Question: Draw a flow chart of sign magnitude addition and subtraction of A & B, where $Q_A = 1$ for addition and $Q_S = 1$ for subtraction, the result stored in A and carry out is stored in E after ALU operation, and A_s and B_s are the sign of A and B respectively.

Twist:

*P - Q or P + Q

* P_s and Q_s are the sign of P and Q

Example

Addition : +6 & +5

-6 & -5


Subtraction : +6 & +5

+5 & +6

-6 & -5


-5 & -6

Rough
 $A - B = A - (+B)$
 $= A + (-B)$

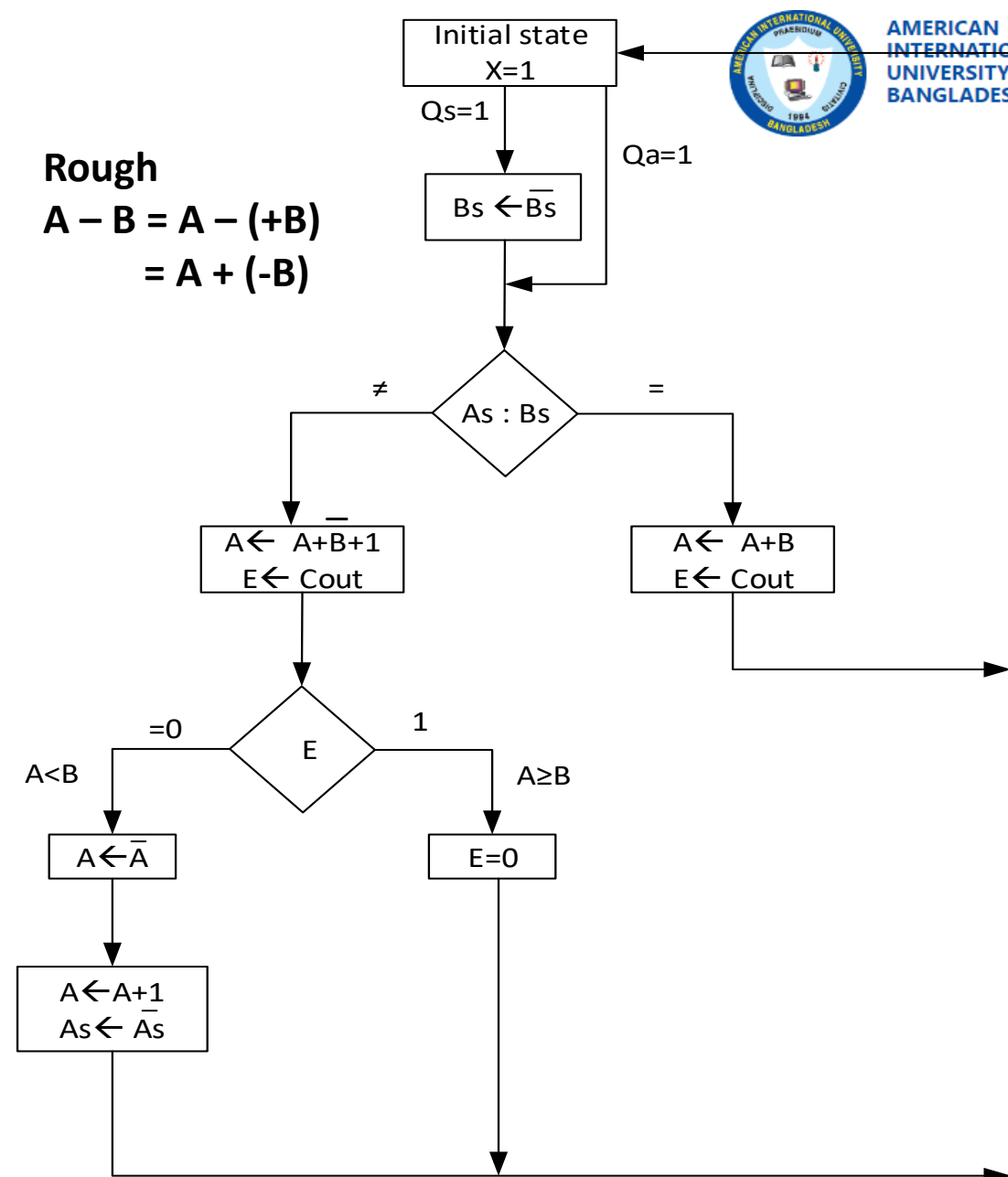

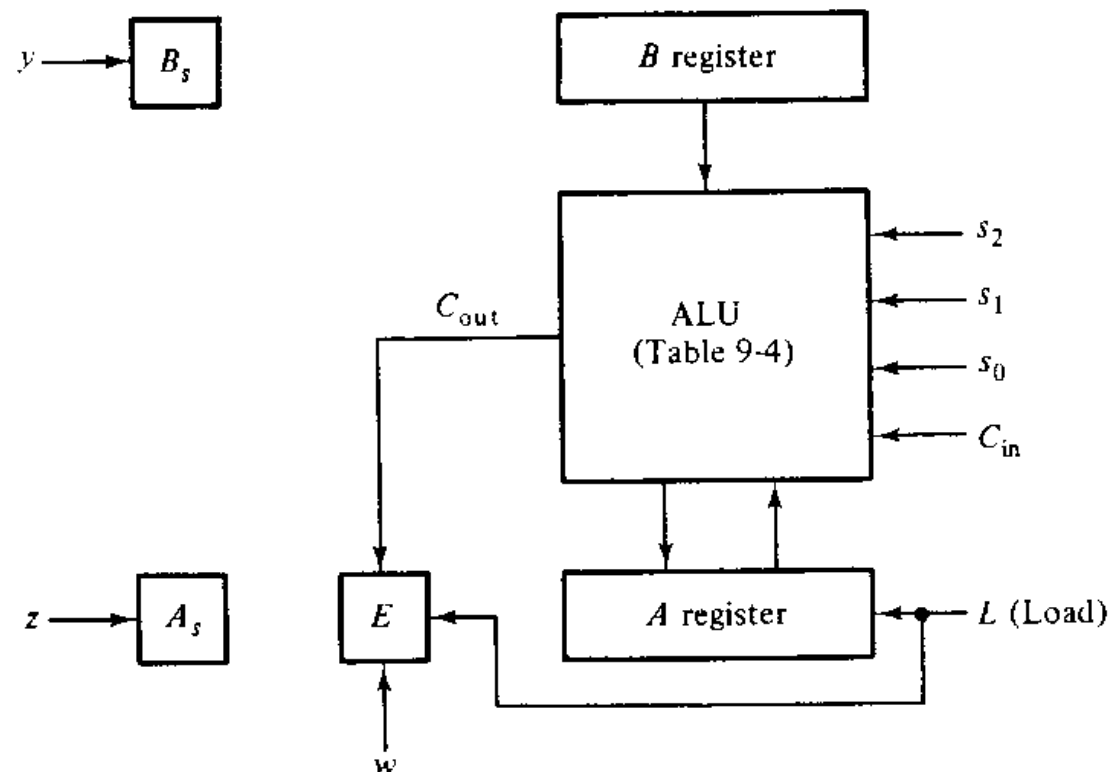4. Data Processor Register


- The operations between A and B can be done with the ALU.
- The operations with A_s , B_s and E must be initiated with separate control variables.




5. Control Block Diagram

- The control receives five inputs: two from the external environment and three from the data-processor.
- To simplify the design, we define new variable S :

$$S = A_s \text{ xor } B_s$$

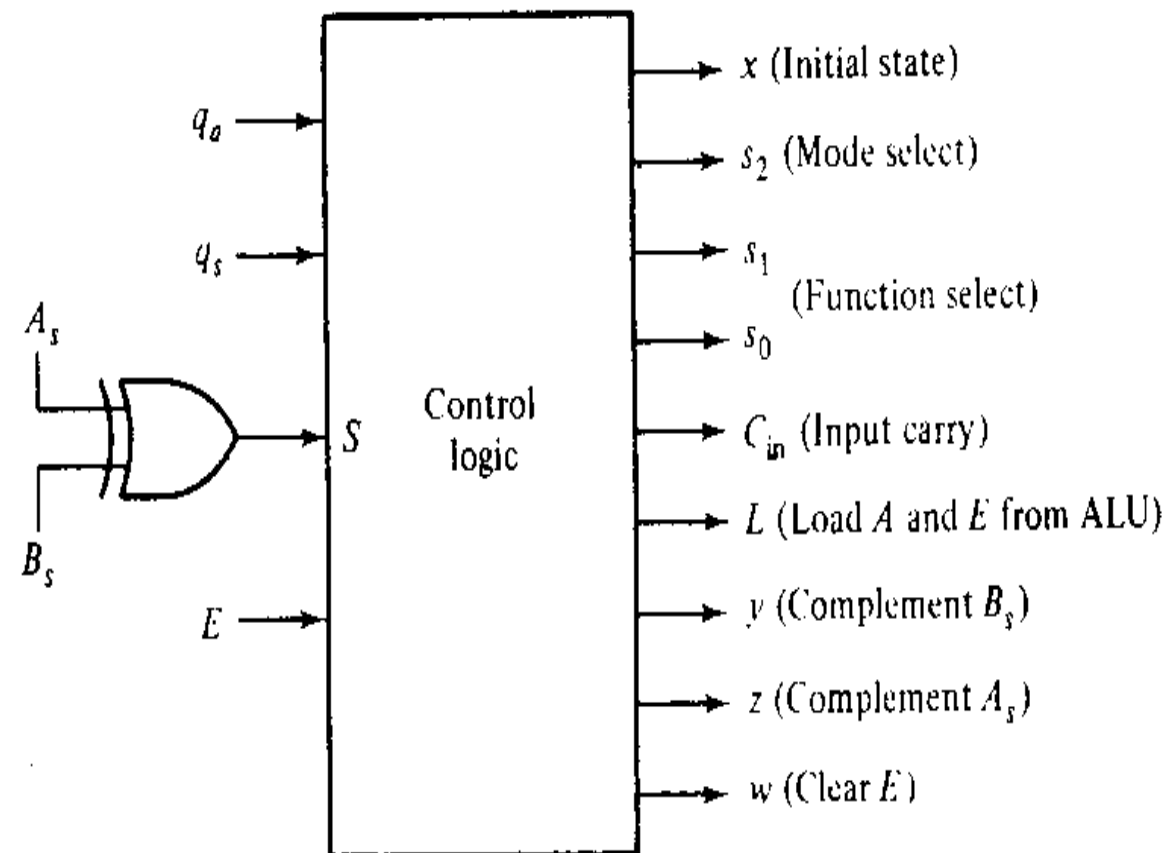


State Diagram and Microinstructions

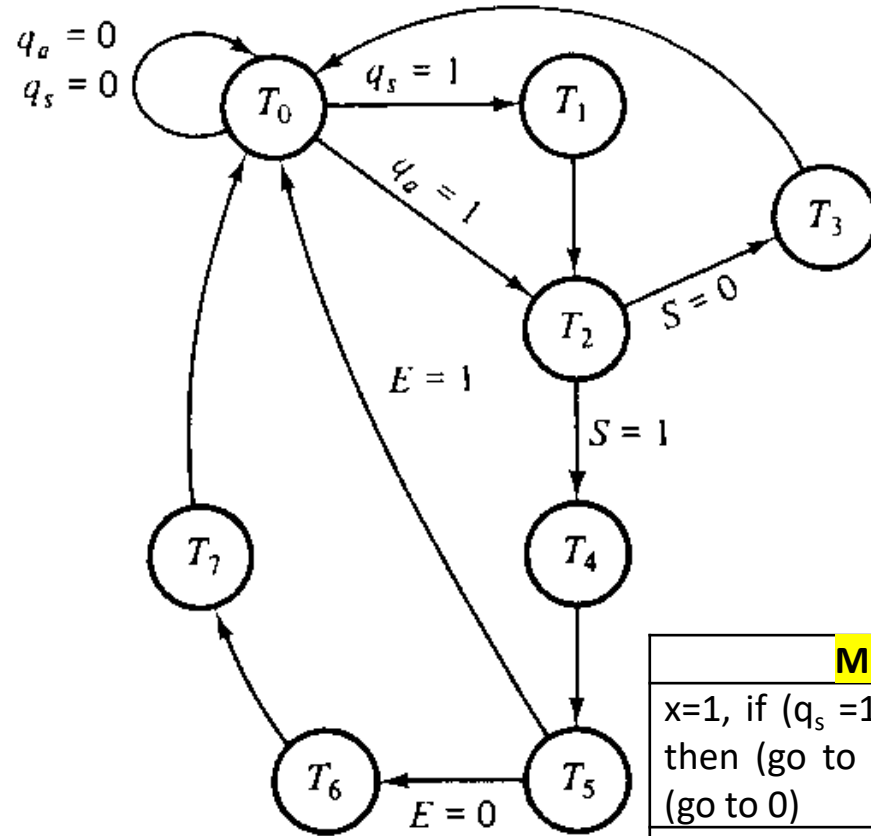

q_a Add
 q_s Subtract
 $S = 0$ Signs alike
 $S = 1$ Signs unlike
 E Output carry

State Diagram

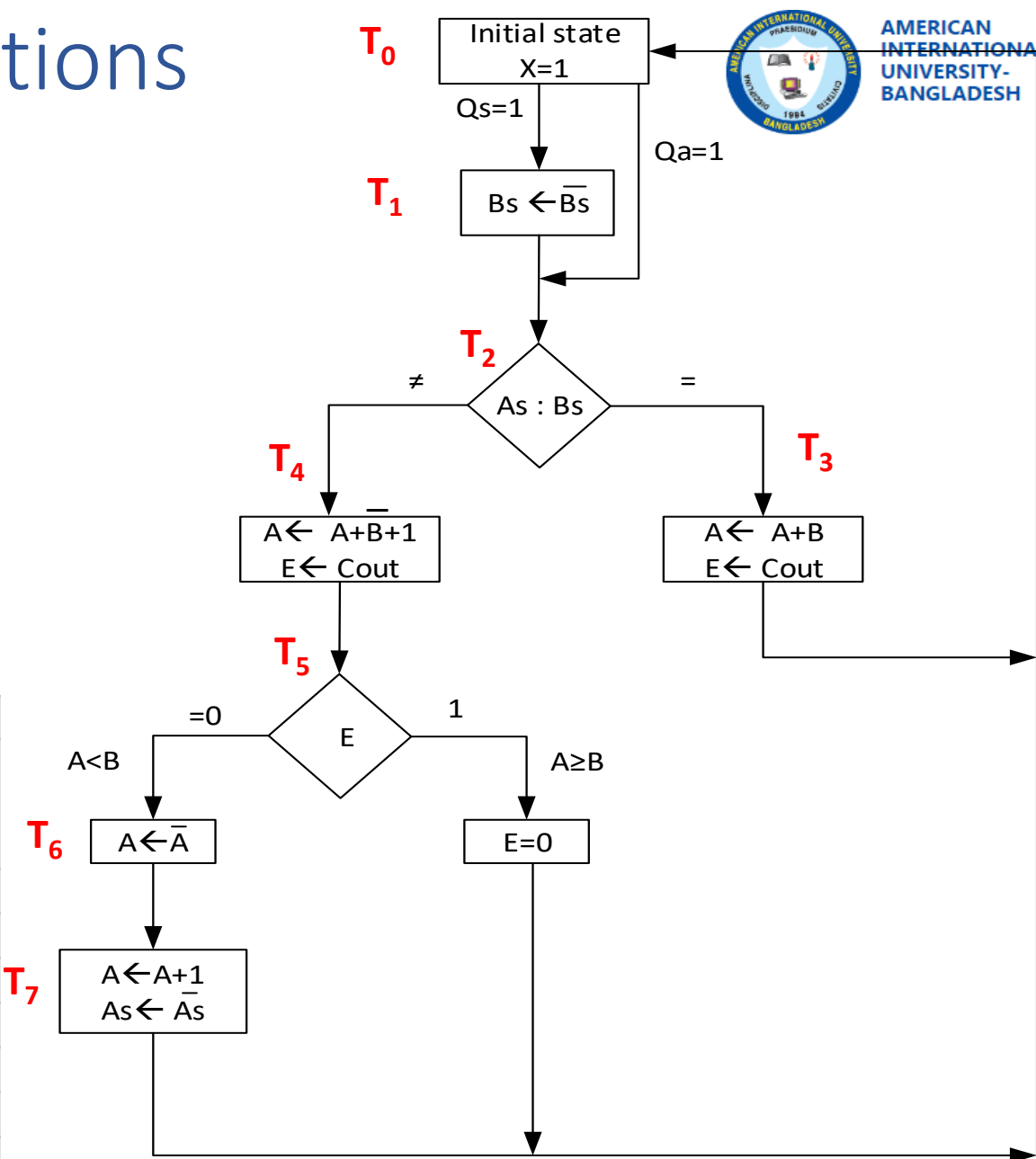Microinstructions
x=1, if ($q_s = 1$) then (go to 1), If ($q_a=1$) then (go to 2), if (q_a and $q_s = 0$) then (go to 0)
$Bs \leftarrow Bs'$
If ($S = 1$), then go to 4
$A \leftarrow A+B$, $E \leftarrow Cout$, go to 0
$A \leftarrow A+B'+1$, $E \leftarrow Cout$
If($E = 1$) then (go to 0), $E \leftarrow 0$
$A \leftarrow A'$
$A \leftarrow A+1$, $As \leftarrow As'$, go to 0



Sequence of register transfers

Boolean Function

$x = T_0$
 $s_2 = T_6$
 $s_1 = T_4 + T_6$
 $s_0 = T_3 + T_6$
 $C_{in} = T_4 + T_7$
 $L = T_3 + T_4 + T_6 + T_7$
 $y = T_1$
 $z = T_7$
 $w = T_5$

Binary code	F with $C_{in} = 0$	F with $C_{in} = 1$
0 0 0	$A, C \leftarrow 0$	$A + 1$
0 0 1	$A + B$	$A + B + 1$
0 1 0	$A - B - 1$	$A - B$
0 1 1	$A - 1$	$A, C \leftarrow 1$
1 0 0	$A \vee B$	—
1 0 1	$A \oplus B$	—
1 1 0	$A \wedge B$	—
1 1 1	\bar{A}	—

T_0 : Initial state $x = 1$

T_1 : $B_s \leftarrow \bar{B}_s$

T_2 : nothing

T_3 : $A \leftarrow A + B$, $E \leftarrow C_{out}$




T_4 : $A \leftarrow A + \bar{B} + 1$, $E \leftarrow C_{out}$

T_5 : $E \leftarrow 0$

T_6 : $A \leftarrow \bar{A}$


T_7 : $A \leftarrow A + 1$, $A_s \leftarrow \bar{A}_s$

Control outputs								
x	s_2	s_1	s_0	C_{in}	L	y	z	w
1	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0
0	0	1	0	1	1	0	0	0
0	0	0	0	0	0	0	0	1
0	1	1	1	0	1	0	0	0
0	0	0	0	1	1	0	1	0

   

To clear 'E', w pin needs to be activated

 Q1. Design control state diagram for the previous flowchart. Develop control outputs for the signals given in following control logic block diagram using the Table and control states you defined.



Binary code	F with $C_{in} = 0$	F with $C_{in} = 1$
0 0 0	$A, C \leftarrow 0$	$A + 1$
0 0 1	$A + B$	$A + B + 1$
0 1 0	$A - B - 1$	$A - B$
0 1 1	$A - 1$	$A, C \leftarrow 1$
1 0 0	$A \vee B$	—
1 0 1	$A \oplus B$	—
1 1 0	$A \wedge B$	—
1 1 1	\bar{A}	—

Flow chart for counting the number of 1's in register R1 and storing in R2.



Example

R1 : 1010 ----- two 1's

R2 : binary of two ---- 010

R1 → Register

R2 → Counter

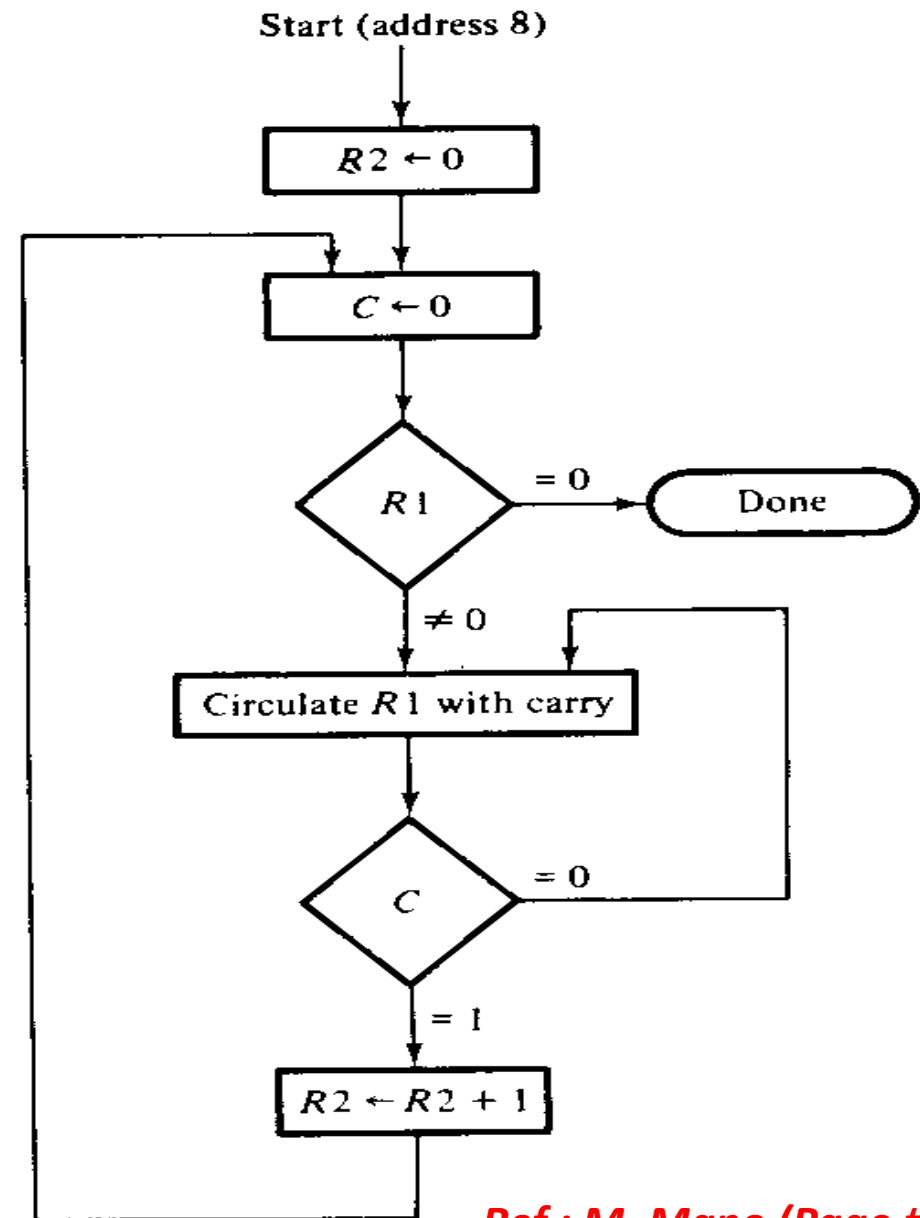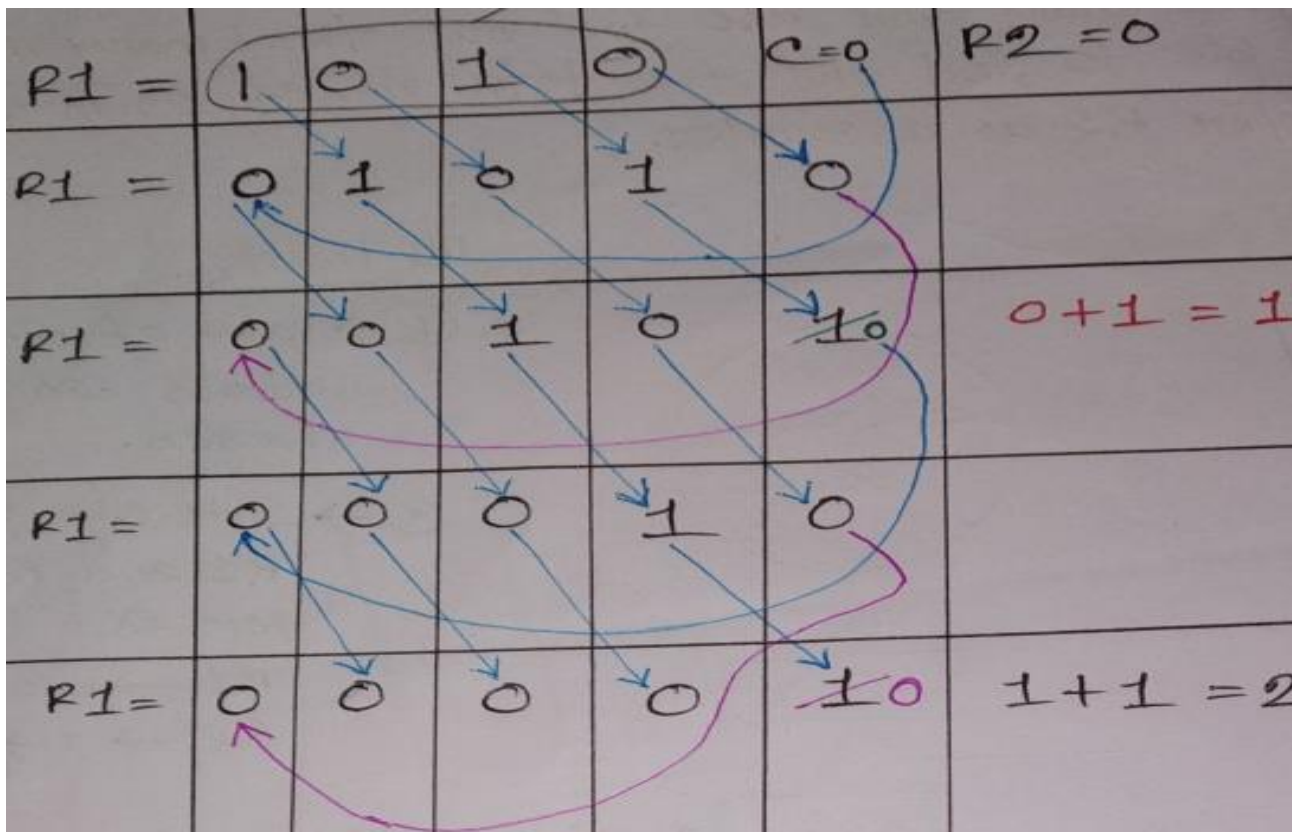

Ref : M. Mano (Page # 432)

Homework



Q1. Draw the flow chart to find out the total number of 1's in register, R1. Use register R2 as counter. [See previous example]

Q2. Draw the flow chart to find out the total number of 1's in register, R2. Use register R1 as counter.

Q3. Draw the flow chart to find out the total number of 0's in register, R1. Use register R2 as counter.

Twist:

***Find total numbers of zeros**

***Register, counter interchanged**